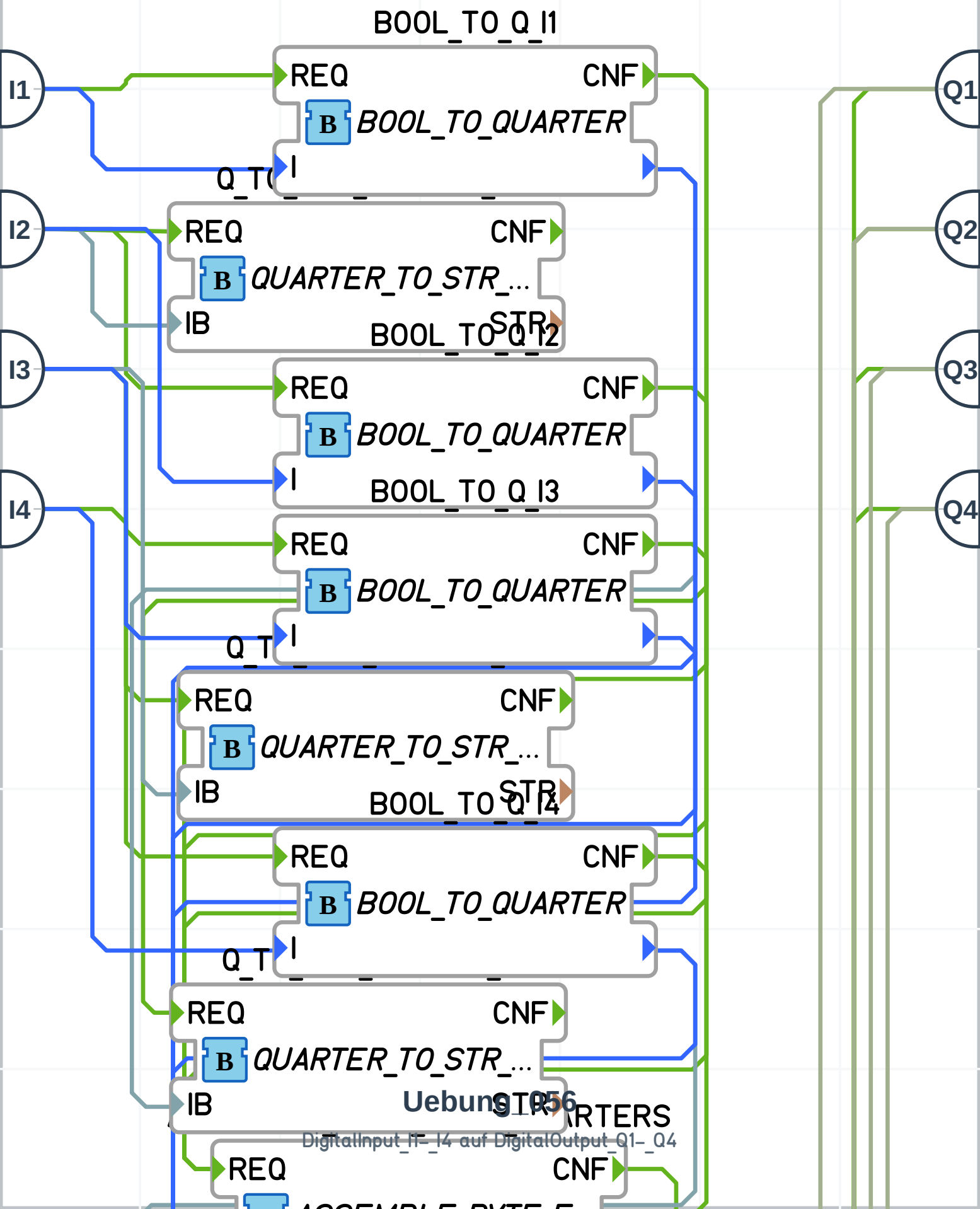
BOOL_TO_Q_I1
I1
REQ
CNF
B
BOOL_TO_QUARTER
I
Q_T
I2
REQ
CNF
B
QUARTER_TO_STR_...
IB
STR
BOOL_TO_Q_I2
I3
REQ
CNF
B
BOOL_TO_QUARTER
I
BOOL_TO_Q_I3
I4
REQ
CNF
B
BOOL_TO_QUARTER
I
Q_T
REQ
CNF
B
QUARTER_TO_STR_...
IB
STR
BOOL_TO_Q_I4
REQ
CNF
B
BOOL_TO_QUARTER
I
Q_T
REQ
CNF
B
QUARTER_TO_STR_...
IB
Uebung
RTERS
DigitalInput_I1_I4 auf DigitalOutput_Q1_Q4
REQ
CNF
Q1
Q2
Q3
Q4